

# Electrical Network Analysis

## Sessional-II Exam

(EE2004)

Total Time (Hrs): 1

Total Marks: 40

Total Questions: 2

Date: November 2<sup>nd</sup>, 2024

Course Instructors

Mr. Abdul Majid

Ms. Beenish Fatima

Mr. Haris Mujtaba

Roll No

Section

Student Signature

Do not write below this line

1. Attempt all the questions.
2. Attempt all parts of the same question together.
3. Show all the steps with proper labelled circuit diagrams, and answers with proper units.


CLO #2: Construct power triangle to compute power in AC circuits.

Q1:

[9 + 3 + 4 + 4 + 5 = 25 marks]

The two loads in the circuit shown below can be described as follows:

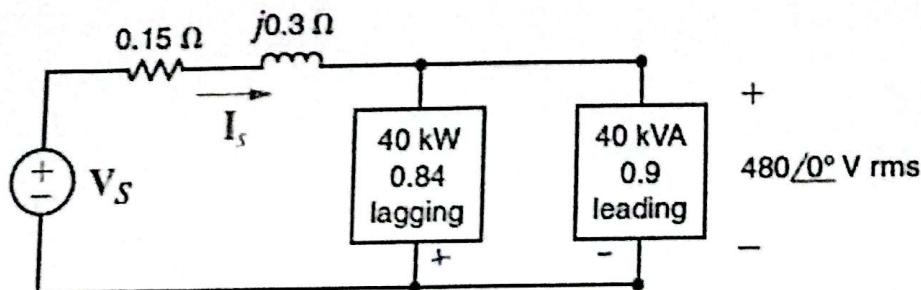Load 1 absorbs an average power of 40kW at a lagging power factor of 0.84 and Load 2 absorbs 40kVA at a leading power factor of 0.9.



- a) Construct the power triangle of each load and compute the total complex power absorbed by the two loads. Determine the power factor of the combined load.
- b) Compute the impedance of the combined load
- c) Compute the current  $I_S$  and the average power loss in the transmission line.
- d) Determine value of source voltage  $V_S$  and the power factor of the source.
- e) Given the frequency of the source is 60Hz, compute the value of the capacitor that will correct the power factor to 1 if placed parallel with the two loads.

CLO #3: Analyze balanced three-phase circuits.

Q2:

[3 + 5 + 3 + 4 = 15 marks]

Analyze a balanced three-phase circuit that has the following characteristics:

- Y-Y connected;
  - The line voltage at the source,  $V_{ab}$ , is  $110\sqrt{3} \angle -60^\circ V_{rms}$ ;
  - The phase sequence is positive (abc);
  - The line impedance is  $3 + j2 \Omega/\phi$ ;
  - The load impedance is  $37 + j28 \Omega/\phi$ ;
- a) Draw the single phase equivalent circuit diagram for the a-phase.
  - b) Calculate all the line currents.
  - c) Calculate all the phase voltages at the load end.
  - d) Calculate the line voltages at the load end.