

CLO #1: Investigate a transformer circuit using Faraday's Law and electric circuit theory

[marks 20]

Q1:

A 60000VA, 4000/230V single phase distribution transformer has series impedance referred to the primary of $12 + j45 \Omega$. The components of the excitation branch referred to the secondary side are $R_c = 50 \Omega$ and $X_M = j 60 \Omega$. Assume a secondary current of 200A with a lagging PF of 0.7547 is provided to a load at rated secondary voltage.

- Draw circuit model referred to secondary side, $\angle \phi$
- Investigate the circuit to find out Voltage regulation
- Find out applied primary voltage
- Find out real power input to the transformer

CLO #1: Investigate a transformer circuit using Faraday's Law and electric circuit theory

[marks 5+5+5+5=20]

Q2:

Draw B-H curve for DC excitation for a ferromagnetic material, clearly indicate knee point, saturation portion and linear portion

Name two types of losses that occur in a transformer's core.

Draw phasor diagram of a transformer for capacitive load

Draw the schematic diagram to perform short circuit test on a transformer.

p