 


**Q1:**

Consider the following circuit




- Construct** the truth table for the function Z.
- Write** the function Z in canonical sum of product form (little m notation).
- Simplify** the function to the minimum number of literals.

**Q2:**

- Design** a combinational multiplier that has two 2-bit inputs  $AA_1A_0$  and  $BB_1B_0$  and 4 bit output  $FF_3FF_2FF_1FF_0$ . **Construct** the truth table and implement it using 4 to 16 line decoder and gates of your choice.

- b) **Construct** the Truth table and write F in  $\Sigma m$  notation.

**Q3:**

 

- a) **Analyze** a sequential circuit with three D flip-flops (A, B, C) defined by the following next state equations

$$\begin{aligned} DD_{AA} &= BB\overline{CC} \\ DD_{BB} &= CC \\ DD_{CC} &= \overline{BB} + XX \end{aligned}$$

Where A, B and C are the outputs of the flip-flops A, B and C respectively, X is the external input and  $DD_{AA}$ ,  $DD_{BB}$  and  $DD_{CC}$  are the input of flip-flops A, B and C respectively. Construct the state table and state diagram of this sequential circuit.

- b) Consider a sequence recognizer circuit that has a serial input S and one output Z. The output becomes one when a sequence 1001 is detected and zero otherwise. **Generate** a state diagram only. Circuit implementation is not required.

**Q4:**

**Design** a synchronous binary arbitrary counter using T Flip-Flop to produce the sequence 1,4,7,3,1 and repeat.

- Construct** the state diagram and state table for the required circuit.
- Construct** the logic diagram of your design using T- flip flops and logic gates.
- Include the unused states in the state diagram and explain if this counter has self correction capability.