


Electronic Devices and Circuits


Metal Oxide Semiconductor Field Effect Transistors (MOSFET)

- Three terminal device
- Source, Drain, Gate
- Basic Operation:
- Voltage between two terminals controls the flow of current in the third terminal
- Applications:
- Amplification, Digital Logic, Memory
- Smaller in size
- Easy to manufacture
- Less power consumption
- MOSFET technology allows the placement of billions of transistor on a single IC
- As compared to BJT, it is more widely used in electronic circuits
- We will study enhancement type MOSFET
- Two types
- N-channel or NMOS
- P-channel or PMOS

N-Channel Enhancement MOSFET

Physical Structure

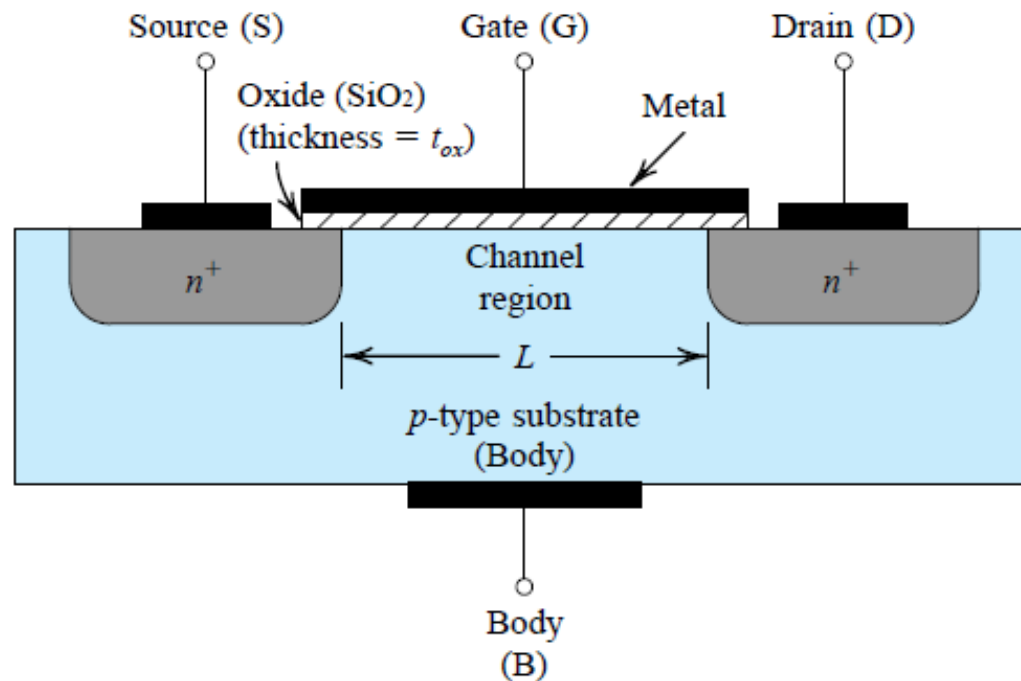

 



 
 


Figure 5.1 Physical structure of the enhancement-type NMOS transistor: **(a)** perspective view; **(b)** cross section. Typically $L = 0.03 \mu\text{m}$ to $1 \mu\text{m}$, $W = 0.1 \mu\text{m}$ to $100 \mu\text{m}$, and the thickness of the oxide layer (t_{ox}) is in the range of 1 to 10 nm.

 

Operation with Zero Gate Voltage

- With zero voltage applied to gate, **two back-to-back diodes** exist in series between drain and source.
- “They” **prevent current conduction** from drain to source when a voltage v_{DS} is applied.
 - yielding very high resistance (10^{12} **ohms**)

 

 


Figure 5.2 The enhancement-type NMOS transistor with a positive voltage applied to the gate. An *n* channel is induced at the top of the substrate beneath the gate.

Creating a Channel for Current Flow

- **Q:** What happens if (1) source and drain are grounded and (2) positive voltage is applied to gate? Refer to figure to right.
 - **step #1:** v_{GS} is applied to the gate terminal, causing a positive build up of positive charge along metal electrode.
 - **step #2:** This “build up” causes free holes to be repelled from region of p -type substrate under gate.

 


Figure : The enhancement-type NMOS transistor with a positive voltage applied to the gate. An n channel is induced at the top of the substrate beneath the gate

Q: What happens if (1) source and drain are grounded and (2) positive voltage is applied to gate? Refer to figure to right.

- **step #3:** This “migration” results in the uncovering of negative bound charges, originally neutralized by the free holes
- **step #4:** The positive gate voltage also **attracts electrons from the n^+ source and drain regions** into the channel.

 


Figure : The enhancement-type NMOS transistor with a positive voltage applied to the gate. An n channel is induced at the top of the substrate beneath the gate

Q: What happens if (1) source and drain are grounded and a positive voltage is applied to gate? Refer to figure to right.

this induced channel is also known as an **inversion layer**

- **step #5:** Once a sufficient number of “these” electrons accumulate, an *n*-region is created...
 - ...connecting the source and drain regions
- **step #6:** This provides path for current flow between *D* and *S*.

 


Figure: The enhancement-type NMOS transistor with a positive voltage applied to the gate. An *n* channel is induced at the top of the substrate beneath the gate

Threshold Voltage

- Represented by V_t
- Data sheet parameter
- minimum value of v_{GS} required to form a conducting channel between drain and source
- V_{tn} is used for n -channel MOSFET, V_{tp} is used for p -channel

Overdrive Voltage (V_{ov})

- The excess of v_{GS} over V_t is called overdrive voltage
- $V_{ov} = V_{GS} - V_t$
- Also called effective voltage

Applying V_{DS} in the presence of V_{GS}

- If $V_{GS} < V_t$,
- No current would flow, cut off
- If $V_{GS} > V_t$
- V_{DS} is small, less than 50mV
- $V_{DS} > 50mV$ but less than V_{ov}
- $V_{DS} > V_{ov}$


MOS Capacitance

- when positive v_{GS} is applied, an **electric field** develops between the gate electrode and induced n -channel – the conductivity of this channel is **affected** by the strength of field
 - SiO_2 layer acts as dielectric
- oxide capacitance** (C_{ox}) – is the **capacitance of the parallel plate capacitor** per unit gate area (F/m^2)

ϵ_{ox} is permittivity of $\text{SiO}_2 = 3.45 \times 10^{-11} (\text{F}/\text{m})$

t_{ox} is thickness of SiO_2 layer
 
$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \text{ in } \text{F}/\text{m}^2$$



Applying small V_{DS}

 


Figure 4.3 An NMOS transistor with $v_{GS} > V_t$ and with a small v_{DS} applied. The device acts as a resistance whose value is determined by v_{GS} . Specifically, the channel conductance is proportional to $v_{GS} - V_t$ and thus i_D is proportional to $(v_{GS} - V_t) v_{DS}$. Note that the depletion region is not shown (for simplicity).

Applying small V_{DS}


- Electrons are emitted from the source and move to drain.
- Direction of conventional current is from drain to source.
- Device acts like a linear resistor whose value is controlled by v_{GS}
- Linear relationship between current and voltage

$$i_D = \left[(\mu_n C_{ox}) \left(\frac{W}{L} \right) v_{OV} \right] v_{DS}$$

$$r_{DS} = \frac{1}{(\mu_n C_{ox}) \left(\frac{W}{L} \right) v_{OV}}$$

$$g_{DS} = (\mu_n C_{ox}) \left(\frac{W}{L} \right) v_{OV}$$

$$r_{DS} = \frac{1}{g_{DS}}$$

 

Applying small V_{DS}

$$i_D = \left[(\mu_n C_{ox}) \left(\frac{W}{L} \right) v_{OV} \right] v_{DS}$$

$$r_{DS} = \frac{1}{(\mu_n C_{ox}) (W/L) v_{OV}}$$

$$r_{DS} = \frac{1}{g_{DS}}$$

$$g_{DS} = (\mu_n C_{ox}) \left(\frac{W}{L} \right) v_{OV}$$

$$k'_n = \mu_n C_{ox}$$

$$k_n = k'_n (W/L)$$

$$k_n = (\mu_n C_{ox}) (W/L)$$

- μ_n = mobility of electrons
- C_{ox} = oxide capacitance
- $\frac{W}{L}$ = aspect ratio
- k'_n = process transconductance parameter
- k_n = MOSFET transconductance parameter

Applying small v_{DS}

- r_{DS} is dependent on three factors
 - process transconductance parameter for NMOS ($\mu_n C_{ox}$) – which is determined by the manufacturing process
 - aspect ratio (W/L) – which is dependent on size requirements / allocations
 - overdrive voltage (v_{OV}) – which is applied by the user

$$r_{DS} = \frac{1}{(\mu_n C_{ox})(W/L)v_{OV}}$$

k_n is known as **NMOS-FET transconductance parameter** and is defined as $\mu_n C_{ox} W/L$


 


Figure : The i_D - v_{DS} characteristics of the MOSFET. when the voltage applied between drain and source V_{DS} is kept small.

The description above indicates that for the MOSFET to conduct, a channel has to be induced. Then, increasing v_{GS} above the threshold voltage V_t enhances the channel, hence the names **enhancement-mode operation** and **enhancement-type MOSFET**. Finally, we note that the current that leaves the source terminal (i_s) is equal to the current that enters the drain terminal (i_D), and the gate current $i_G = 0$.

Effect of V_{ov} on channel

 
- As v_{ov} grows, so does the **depth of the n -channel** as well as its conductivity



Operation as v_{DS} is increased

$$v_{DS} < V_{OV}$$

 - Current voltage relationship is no longer linear
- Triode region



$$i_D = k'_n \left(\frac{W}{L} \right) \left(V_{OV} - \frac{1}{2} v_{DS} \right) v_{DS}$$


$$i_D = k'_n \left(\frac{W}{L} \right) \left(V_{OV} v_{DS} - \frac{1}{2} v_{DS}^2 \right)$$


Figure 5.5 Operation of the enhancement NMOS transistor as v_{DS} is increased. The induced channel acquires a tapered shape, and its resistance increases as v_{DS} is increased. Here, v_{GS} is kept constant at a value $> V_t$; $v_{GS} = V_t + V_{OV}$.

Operation as $v_{DS} \geq V_{ov}$

- Current becomes constant
- Channel pinch off occurs
- MOSFET enters the saturation region
- Used as a voltage controlled current source.
- MOS is used as an amplifier
- Drain current is dependent on V_{GS} and independent of V_{DS}
 
$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) V_{OV}^2$$




 

$$i_D = \begin{cases} \text{triode: } (\mu_n C_{ox}) \frac{W}{L} \left(v_{OV} - \frac{1}{2} v_{DS} \right) v_{DS} & \text{if } v_{DS} < v_{OV} \\ \text{saturation: } \frac{1}{2} (\mu_n C_{ox}) \frac{W}{L} v_{OV}^2 & \text{otherwise} \end{cases}$$

Figure 4.6 The drain current i_D versus the drain-to-source voltage v_{DS} for an enhancement-type NMOS transistor operated with $v_{GS} > V_t$.

The i_D - v_{DS} Characteristics

 

 


Figure 4.10 (a) Circuit symbol for the n -channel enhancement-type MOSFET. (b) Modified circuit symbol with an arrowhead on the source terminal to distinguish it from the drain and to indicate device polarity (i.e., n channel). (c) Simplified circuit symbol to be used when the source is connected to the body or when the effect of the body on device operation is unimportant.


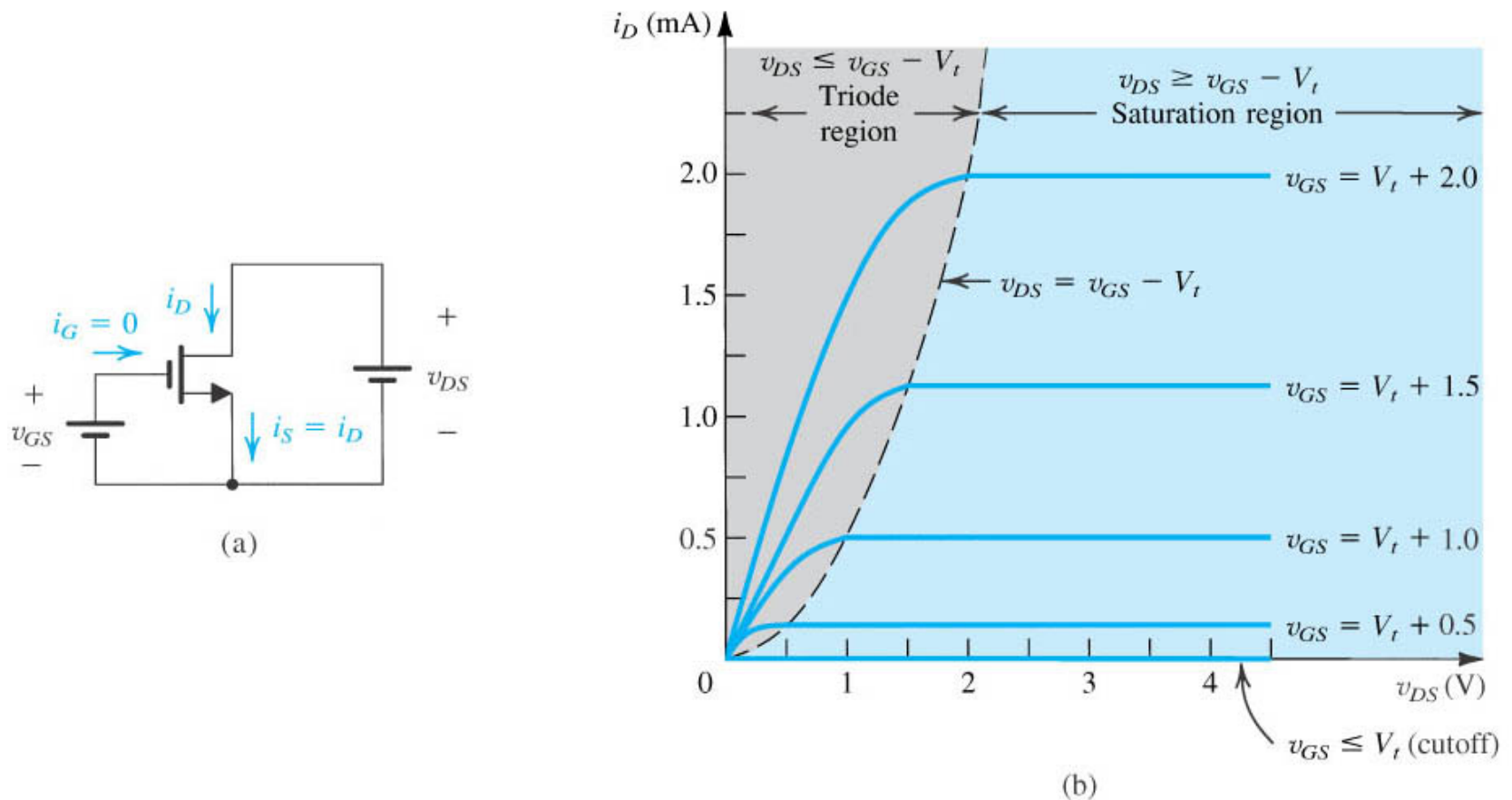
 
 


Figure 4.11 (a) An n -channel enhancement-type MOSFET with v_{GS} and v_{DS} applied and with the normal directions of current flow indicated. (b) The i_D - v_{DS} characteristics for a device with $k'_n (W/L) = 1.0 \text{ mA/V}^2$.

Effect of v_{DS} on the shape of channel

- v_{DS} is small
- channel is uniform
- $v_{DS} < V_{ov}$
- Channel is tapered
- $v_{DS} \geq V_{ov}$
- Channel is pinched off

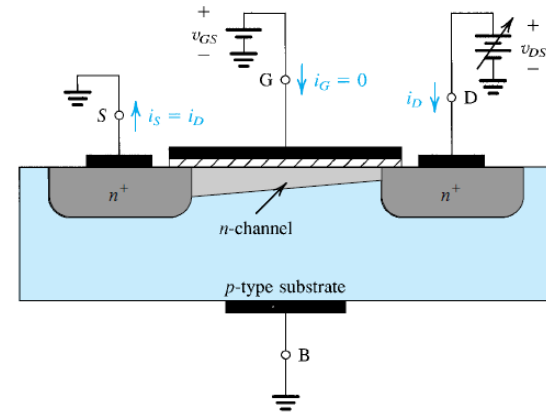


 


 


Figure 4.7 Increasing v_{DS} causes the channel to acquire a tapered shape. Eventually, as v_{DS} reaches $v_{GS} - V_t$ the channel is pinched off at the drain end. Increasing v_{DS} above $v_{GS} - V_t$ has little effect (theoretically, no effect) on the channel's shape.

Reason for non uniform channel

- Understand two parameters
 1. Voltage drop across channel from drain to source v_{DS}
 2. Voltage difference between gate and channel v_{GD}




Reason for non uniform channel


- $v_{GD} = v_{GS} - v_{DS}$
- $v_{DS} > v_{GS} - V_t$  Condition for saturation
- $v_D - v_S > v_G - v_S - V_t$
- $v_D > v_G - V_t$
- $v_D - v_G > -V_t$
- $v_{DG} > -V_t$
- $-v_{GD} > -V_t$
- $v_{GD} < V_t$
- $v_{GD} > V_t$  Triode Region
- $v_{GD} = v_{GS} - (v_{GS} - V_t) = V_t$  Edge of saturation

Reason for non uniform channel

- v_{GS} is held constant at value greater than V_t .
- v_{DS} is applied and appears as voltage drop across the length of the n -channel.
- At the source end:
 - $V_{GD} = V_{GS}$
- At the drain end:
 - $V_{GD} = V_{GS} - V_{DS}$
 - Going from drain to source, voltage drop at each point with respect to source decreases linearly.
- For small values of v_{DS} , one can still assume that voltage between gate and n -channel is constant

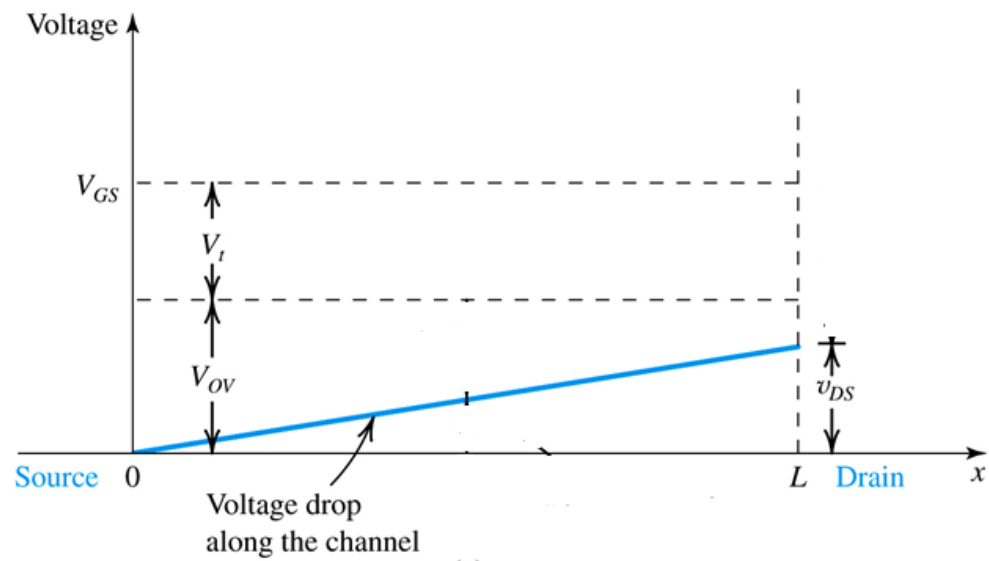

(a)

 

(b)


 


Figure : Operation of MOSFET with $v_{GS} = V_t + v_{OV}$ as v_{DS} is increased to v_{OV} . At the drain end, v_{GD} decreases to V_t and the channel depth at the drain-end reduces to zero (pinch-off). At this point, the MOSFET enters saturation mode of operation. Further increasing v_{DS} (beyond v_{OV}) has no effect on the channel shape and i_D remains constant.

Table 5.1 Regions of Operation of the Enhancement NMOS Transistor

 

- $v_{GS} < V_{in}$: no channel; transistor in cut-off; $i_D = 0$
- $v_{GS} = V_{in} + v_{OV}$: a channel is induced; transistor operates in the triode region or the saturation region depending on whether the channel is continuous or pinched-off at the drain end;

Triode Region

Continuous channel, obtained by:

$$v_{GD} > V_{in}$$

or equivalently:

$$v_{DS} < v_{OV}$$

Then,

$$i_D = k'_n \left(\frac{W}{L} \right) \left[(v_{GS} - V_{in}) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

or equivalently,

$$i_D = k'_n \left(\frac{W}{L} \right) \left(v_{OV} - \frac{1}{2} v_{DS} \right) v_{DS}$$

Saturation Region

Pinched-off channel, obtained by:

$$v_{GD} \leq V_{in}$$

or equivalently:

$$v_{DS} \geq v_{OV}$$

Then

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{GS} - V_{in})^2$$

or equivalently,

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) v_{OV}^2$$

Consider a process technology for which $L_{\min} = 0.4 \mu\text{m}$, $t_{ox} = 8 \text{ nm}$, $\mu_n = 450 \text{ cm}^2/\text{V}\cdot\text{s}$, and $V_t = 0.7 \text{ V}$.

(a) Find C_{ox} and k'_n .

(b) For a MOSFET with $W/L = 8 \mu\text{m}/0.8 \mu\text{m}$, calculate the values of V_{OV} , V_{GS} , and $V_{DS\min}$ needed to operate the transistor in the saturation region with a dc current $I_D = 100 \mu\text{A}$.

(c) For the device in (b), find the values of V_{OV} and V_{GS} required to cause the device to operate as a $1000\text{-}\Omega$ resistor for very small v_{DS} .

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{8 \times 10^{-9}} = 4.32 \times 10^{-3} \text{ F/m}^2 = 4.32 \text{ fF}/\mu\text{m}^2$$

$$V_{GS} = V_t + V_{OV} = 1.02 \text{ V}$$

$$V_{DS\min} = V_{OV} = 0.32 \text{ V}$$

$$k'_n = \mu_n C_{ox} = 450 (\text{cm}^2/\text{V}\cdot\text{s}) \times 4.32 (\text{fF}/\mu\text{m}^2)$$

$$= 450 \times 10^8 (\mu\text{m}^2/\text{V}\cdot\text{s}) \times 4.32 \times 10^{-15} (\text{F}/\mu\text{m}^2)$$

$$= 194 \times 10^{-6} (\text{F}/\text{V}\cdot\text{s})$$

$$= 194 \mu\text{A}/\text{V}^2$$

(c) For the MOSFET in the triode region with v_{DS} very small,

$$r_{DS} = \frac{1}{k'_n \frac{W}{L} V_{OV}}$$

$$1000 = \frac{1}{194 \times 10^{-6} \times 10 \times V_{OV}}$$

$$V_{OV} = 0.52 \text{ V}$$

$$V_{GS} = 1.22 \text{ V}$$

(b) For operation in the saturation region,

$$i_D = \frac{1}{2} k'_n \frac{W}{L} v_{OV}^2$$

$$100 = \frac{1}{2} \times 194 \times \frac{8}{0.8} V_{OV}^2$$

$$V_{OV} = 0.32 \text{ V}$$

Consider an NMOS transistor fabricated in a 0.18- μm process with $L = 0.18\text{ }\mu\text{m}$ and $W = 2\text{ }\mu\text{m}$. The process technology is specified to have $C_{ox} = 8.6\text{ fF}/\mu\text{m}^2$, $\mu_n = 450\text{ cm}^2/\text{V}\cdot\text{s}$, and $V_{tn} = 0.5\text{ V}$.

- Find V_{GS} and V_{DS} that result in the MOSFET operating at the edge of saturation with $I_D = 100\text{ }\mu\text{A}$.
- If V_{GS} is kept constant, find V_{DS} that results in $I_D = 50\text{ }\mu\text{A}$.
- To investigate the use of the MOSFET as a linear amplifier, let it be operating in saturation with $V_{DS} = 0.3\text{ V}$. Find the change in i_D resulting from v_{GS} changing from 0.7 V by $+0.01\text{ V}$ and by -0.01 V .

$$\begin{aligned} k'_n &= \mu_n C_{ox} \\ &= 450 \times 10^{-4} \times 8.6 \times 10^{-15} \times 10^{12}\text{ A/V}^2 \\ &= 387\text{ }\mu\text{A/V}^2 \end{aligned}$$

$$\begin{aligned} k_n &= k'_n \left(\frac{W}{L} \right) \\ &= 387 \left(\frac{2}{0.18} \right) = 4.3\text{ mA/V}^2 \end{aligned}$$

$$I_D = \frac{1}{2} k_n V_{OV}^2$$

$$100 = \frac{1}{2} \times 4.3 \times 10^3 \times V_{OV}^2$$

$$V_{OV} = 0.22\text{ V}$$

$$V_{GS} = V_{tn} + V_{OV} = 0.5 + 0.22 = 0.72\text{ V}$$

$$V_{DS} = V_{OV} = 0.22\text{ V}$$

$$I_D = k_n \left[V_{OV} V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$50 = 4.3 \times 10^3 \left[0.22 V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$V_{DS}^2 - 0.44 V_{DS} + 0.023 = 0$$

$$V_{DS} = 0.06\text{ V} \quad \text{and} \quad V_{DS} = 0.39\text{ V}$$

$$V_{DS} = 0.06\text{ V}$$

$$\text{For } v_{GS} = 0.7\text{ V}, V_{OV} = 0.2\text{ V},$$

since $V_{DS} = 0.3\text{ V}$, the transistor is operating in saturation and

$$\begin{aligned} I_D &= \frac{1}{2} k_n V_{OV}^2 \\ &= \frac{1}{2} \times 4300 \times 0.04 \\ &= 86\text{ }\mu\text{A} \end{aligned}$$

$$\text{Now for } v_{GS} = 0.710\text{ V}, v_{OV} = 0.21\text{ V},$$

$$i_D = \frac{1}{2} \times 4300 \times 0.21^2 = 94.8\text{ }\mu\text{A}$$

$$\text{for } v_{GS} = 0.690\text{ V}, v_{OV} = 0.19\text{ V},$$

$$i_D = \frac{1}{2} \times 4300 \times 0.19^2 = 77.6\text{ }\mu\text{A}$$

$$\Delta V_{GS} = +0.01\text{ V}, \Delta i_D = 8.8\text{ }\mu\text{A};$$

$$\Delta V_{GS} = -0.01\text{ V}, \Delta i_D = -8.4\text{ }\mu\text{A}.$$

We conclude that the two changes are almost equal, an indication of almost-linear operation when the changes in v_{GS} are kept small. This is just a preview of the “small-signal operation” of the MOSFET stud-

Design the circuit of Fig. 5.21, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5 \text{ V}$. The NMOS transistor has $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, $L = 1 \mu\text{m}$, and $W = 32 \mu\text{m}$. Neglect the channel-length modulation effect (i.e., assume that $\lambda = 0$).

$$R_D = \frac{V_{DD} - V_D}{I_D} \\ = \frac{2.5 - 0.5}{0.4} = 5 \text{ k}\Omega$$

$$V_G = 0$$

$$V_{GD} = 0 - 0.5$$

$$V_{GD} < V_t$$

Device in saturation


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$

substituting $I_D = 0.4 \text{ mA} = 400 \mu\text{A}$, $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, and $W/L = 32/1$

$$400 = \frac{1}{2} \times 100 \times \frac{32}{1} V_{OV}^2$$

$$V_{OV} = 0.5 \text{ V}$$
 
$$V_{GS} = V_t + V_{OV} = 0.7 + 0.5 = 1.2 \text{ V}$$



the source must be at -1.2 V

$$R_S = \frac{V_S - V_{SS}}{I_D}$$

$$= \frac{-1.2 - (-2.5)}{0.4}$$

$$= 3.25 \text{ k}\Omega$$

Design the circuit in Fig. 5.23 to establish a drain voltage of 0.1 V. What is the effective resistance between drain and source at this operating point? Let $V_{tn} = 1$ V and $k'_n(W/L) = 1$ mA/V².

$$V_G = +5V$$

$$V_D = 0.1V$$

$$V_{GD} = 5 - 0.1$$

$$V_{GD} > V_t$$


Device in triode region

$$I_D = k'_n \frac{W}{L} \left[(V_{GS} - V_{tn}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\begin{aligned} I_D &= 1 \times \left[(5 - 1) \times 0.1 - \frac{1}{2} \times 0.01 \right] \\ &= 0.395 \text{ mA} \end{aligned}$$

$$\begin{aligned} R_D &= \frac{V_{DD} - V_D}{I_D} \\ &= \frac{5 - 0.1}{0.395} = 12.4 \text{ k}\Omega \end{aligned}$$
 
$$r_{DS} = \frac{V_{DS}}{I_D} = \frac{0.1}{0.395} = 253 \text{ }\Omega$$



Analyze the circuit shown in Fig. 5.24(a) to determine the voltages at all nodes and the currents through all branches. Let $V_{tn} = 1 \text{ V}$ and $k'_n(W/L) = 1 \text{ mA/V}^2$. Neglect the channel-length modulation effect (i.e., assume $\lambda = 0$).

$$V_G = V_{DD} \frac{R_{G2}}{R_{G2} + R_{G1}} = 10 \times \frac{10}{10 + 10} = +5 \text{ V}$$


$$I_G = 0$$

Assume the device in saturation mode

$$V_D = V_{DD} - I_D R_D$$

$$I_D = I_S$$

$$V_S = I_D R_S$$

 

$$V_{GS} = 5 - 6I_D$$

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_{tn})^2$$

$$= \frac{1}{2} \times 1 \times (5 - 6I_D - 1)^2$$

$$18I_D^2 - 25I_D + 8 = 0$$


$$I_D: 0.89 \text{ mA and } 0.5 \text{ mA.}$$

$$V_S = 0.89 \times 6$$

$$V_S = 5.34 \text{ V}$$

$$V_{GS} = 5 - 5.34$$

Negative V_{GS} is not valid for NMOS

 

$$I_D = 0.5 \text{ mA}$$

$$V_S = 0.5 \times 6 = +3 \text{ V}$$

$$V_{GS} = 5 - 3 = 2 \text{ V}$$

$$V_D = 10 - 6 \times 0.5 = +7 \text{ V}$$

$$V_{GD} = 5 - 7$$

the transistor is operating in saturation, as initially assumed.