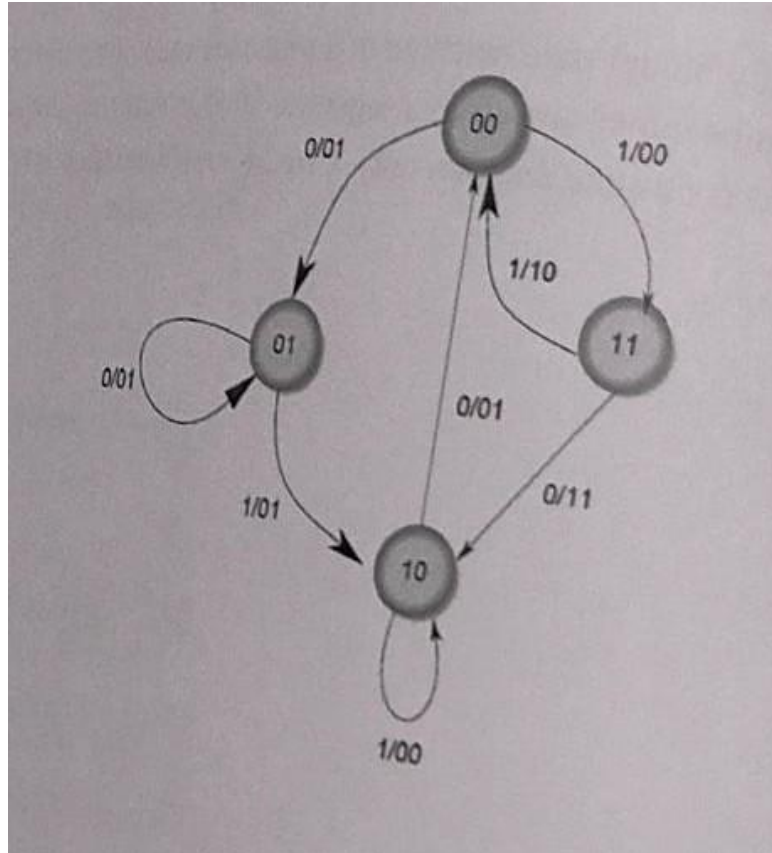


**Q1:** Convert the following state diagram into state table and implement the circuit using JK Flip Flops



**Q3:** Tables in a restaurant are labeled A to D. Where customers are settled, they ring a bell placed on center of table to call waiter. Waiter gets to know when bulb indicating specific table gets **ON**. If more than two tables are ON simultaneously then priority is given in the following order to serve the customer.

Priority of table **D** > Priority of table **A** > Priority of table **C** > Priority of table **B**

You are required to design a circuit for the restaurant that helps them decide which customer to serve currently. The circuit must have three outputs (**E, F, G**). If the customer is not to be served then **E=0**, otherwise **E=1**. **F & G** indicates the table to be served.

**Codes are:**

Table	Code
A	00
B	01
C	10
D	11

- Show Truth Table for outputs E, F, and G.
- Find minimal SOP and POS expression for each output using **K-maps**.

**Q4:** Design a digital circuit to check whether the inequalities  $3x+2>24$  and  $3x+6>37$  are true or not. Here, x is unsigned 4-bit number.

- Implement using  $8 \times 1$  mux when x1, x2 and x4 are selection bits.
- Implement using  $4 \times 1$  mux when x1 and x3 are selection bits.

**Q5:** Design a MN flip flop with following characteristics:

If **MN 00**, the next state of the flip-flop is **0**.

If **MN 01**, the next state of the flip-flop is same as present state.

If **MN 10**, the next state of the flip-flop is the complement of the present state.

If **MN 11**, the next state of the flip-flop is **1**.

- Write State Table
- Compute following excitation table for MN flip flop (use don't cares where necessary)

Present State Q(t)	Next State Q(t+1)	M	N
0	0		
0	1		
1	0		
1	1		

- Derive the characteristic equation/ next State equation
- Draw state diagram
- Draw circuit diagram using JK-flip-flop and logic gates.

**Q6:** Design the following circuit that performs the following operations on A (3-bit number) according to the status of selection bit S:

<b>S</b>	<b>Operation</b>	<b>F (Output)</b>
<b>0</b>	Incrementor	$A+1$
<b>1</b>	Tripler	$3*A$