

Linear Circuit Analysis

(EE1001)

Date: June 3rd, 2024

Course Instructor(s)

Dr. Saima Zafar

Mohsin Yousuf

Beenish Fatima (CM)

Akbare Yaqoob

Final Exam

Total Time (Hrs):

3

Total Marks:

50

Total Questions:

5

Roll No

Section

Student Signature

Do not write below this line

1. Attempt all the questions.
2. Attempt all parts of the same question together.
3. Show all the steps with proper circuit diagrams, and answers with proper units.


CLO # 2: Apply DC circuit analysis techniques and theorems to solve linear resistive circuits.

Q1:

[10 marks]

- a) Solve the circuit below to determine the Thévenin Equivalent w.r.t. terminals 'a' and 'b'.
Construct the Thévenin Equivalent circuit [6 marks]
- b) If a load resistor R_L is connected between terminals 'a' and 'b', determine the value of R_L for maximum power transfer. [2 marks]
- c) Calculate the maximum power delivered to R_L . [2 marks]

$$P_{max} = \frac{V_{th}^2}{4R}$$

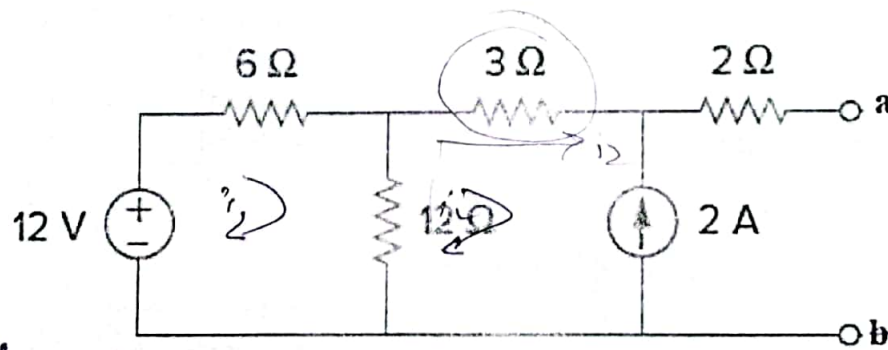

$$P_{max} = \frac{36.06^2}{4 \times 2} = 36.062$$

CLO # 3: Solve circuits containing ideal operational amplifiers


Q2:

[10 marks]

- Solve the circuit to determine the expression for v_o in terms of v_s and the type of op-amp configuration. [5 marks]
- Calculate v_o if v_s is replaced by a -3V source. [2 marks]
- Determine the range of values for v_s such that v_o does not saturate and the op-amp remains in its linear region of operation. [3 marks]

$$V_o = 15 + 2V_s$$

$$V_o = 9V \rightarrow (-3) - v_s$$

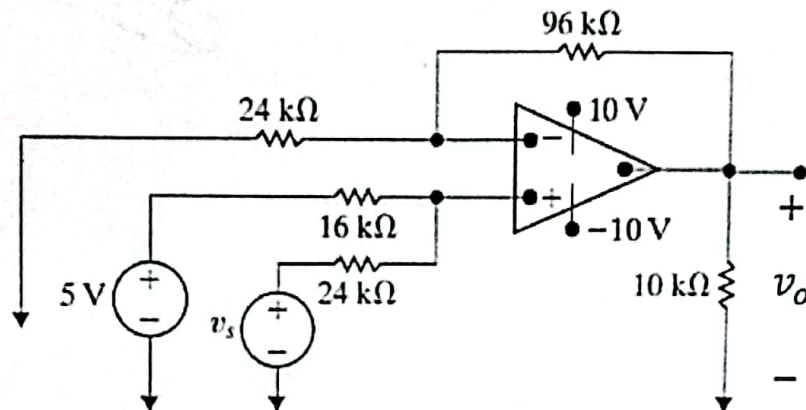


CLO # 4: Analyze natural and step response of circuits containing R, L, and C

Q3:

[10 marks]

The current in the two capacitors shown below is $500 e^{-200t}$ mA for $t \geq 0$. The initial values of v_1 and v_2 are 15 V and -10 V, respectively. Figure out the following

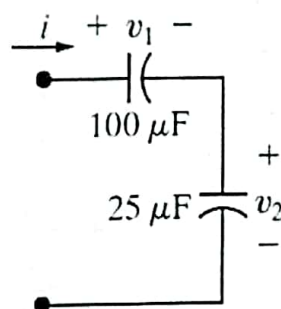- Equivalent capacitance [2 marks]
- Initial energy stored in each capacitor [2 marks]
- $v_1(t)$ and $v_2(t)$ for $t \geq 0$ [4 marks]
- Final energy in each capacitor, as $t \rightarrow \infty$ [2 marks]



National University of Computer and Emerging Sciences Lahore Campus


CLO # 4: Analyze natural and step response of circuits containing R, L, and C

[10 marks]

Q4:

The switch in the circuit shown below has been in position *b* for a long time. At $t = 0$, the switch moves from position *b* to position *a*. Identify the type of response and figure out the following quantities:

- | | | | |
|----|--------------------|--|-----------|
| a) | $i(0^+)$ | <u>0</u> | [2 marks] |
| b) | $v(0^+)$ | <u>24</u> | [2 marks] |
| c) | $\tau, t > 0$ | <u>20 ms</u> | [2 marks] |
| d) | $i(t), t \geq 0$ | <u>0 A</u> | [2 marks] |
| e) | $v(t), t \geq 0^+$ | <u>$24 e^{-t/0.02} \text{ V}$</u> | [2 marks] |

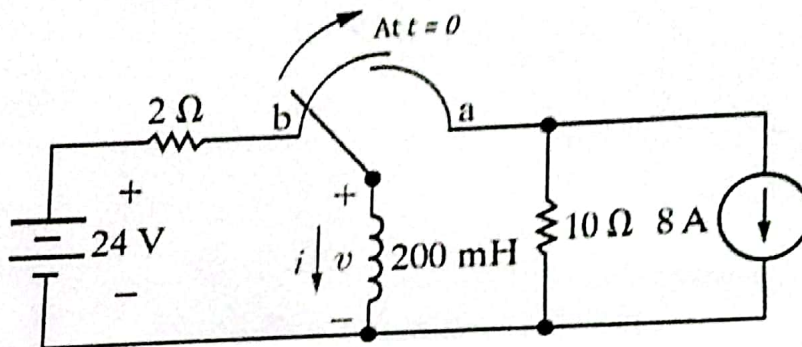

$\frac{di}{dt}$
 i
 v

CLO # 2: Apply DC circuit analysis techniques and theorems to solve linear resistive circuits.

[10 marks]

Q5:

- Apply the node voltage method to determine voltages at all essential nodes.
- Calculate the power associated with both dependent sources.

[7 marks]

[3 marks]

